



భారతీయ సాంకేతిక విజ్ఞాన సంస్థ హైదరాబాద్
भारतीय प्रौद्योगिकी संस्थान हैदराबाद
Indian Institute of Technology Hyderabad

Year : 2023-24
Subject Code : EE1200
Branch : Electrical Engineering
Name : Aditi Dure


Verification of KCL and KVL

1 Aim

To verify Kirchhoff's Voltage Law (KVL) and Kirchhoff's Current Law (KCL) in the given circuit

2 Circuit Diagram

2.1 KCL:

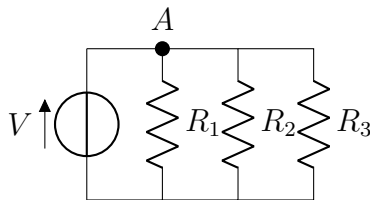

where


$$V = 5V \quad (1)$$

$$R_1 = 100\Omega \quad (2)$$

$$R_2 = 220\Omega \quad (3)$$

$$R_2 = 180\Omega \quad (4)$$

2.2 KVL:

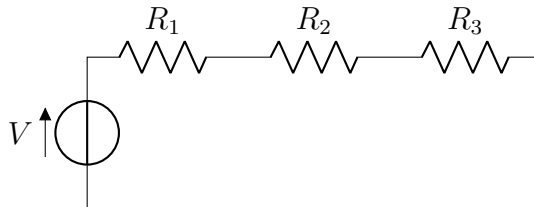

where

$$V = 5V \quad (5)$$

$$R_1 = 100\Omega \quad (6)$$

$$R_2 = 220\Omega \quad (7)$$

$$R_2 = 180\Omega \quad (8)$$

3 Theory

KCL:

At any node in an electrical circuit, the net current is zero.

KVL:

In closed path of an electrical circuit the net potential around the closed path is zero.

4 Theoretical calculations:

4.1 For verifying KCL:

Applying KCL at node A:

To find I,

$$I = I_1 + I_2 + I_3 \quad (9)$$

$$R_{eq} = \left(\frac{1}{100} + \frac{1}{180} + \frac{1}{220} \right)^{-1} \quad (10)$$

$$R_{eq} = 49.74 \, \Omega \quad (11)$$

$$I = \frac{V}{R_{eq}} \quad (12)$$

$$I = \frac{5}{49.74} \quad (13)$$

$$I = 0.1 \, \text{A} \quad (14)$$

To find I_1 , I_2 , I_3 using current division rule:

$$I_1 = \frac{100 \cdot I}{100 + 220 + 180} = 0.02 \, \text{A} \quad (15)$$

$$I_2 = \frac{220 \cdot I}{100 + 220 + 180} = 0.044 \, \text{A} \quad (16)$$

$$I_3 = \frac{180 \cdot I}{100 + 220 + 180} = 0.036 \, \text{A} \quad (17)$$

4.2 For verifying KVL:

Assume current's direction to be clockwise

Applying KVL in loop:

Assume the current to be I,

$$-V + I \cdot R_1 + I \cdot R_2 + I \cdot R_3 = 0 \quad (18)$$

$$-5 + I \cdot 100 + I \cdot 220 + I \cdot 180 = 0 \quad (19)$$

On solving, we get

$$I = 0.01 \, \text{A} \quad (20)$$

so,

$$\begin{aligned}V_1 &= I \cdot R_1 = 0.01 \text{ A} \cdot 100 \Omega = 1 \text{ V} \\V_2 &= I \cdot R_2 = 0.01 \text{ A} \cdot 220 \Omega = 2.2 \text{ V} \\V_3 &= I \cdot R_3 = 0.01 \text{ A} \cdot 180 \Omega = 1.8 \text{ V}\end{aligned}$$

5 Observation

5.1 For KCL:

	theoretical	practical
I(A)	0.1A	0.09A
I_1 (A)	0.02A	0.019A
I_2 (A)	0.044A	0.045A
I_3 (A)	0.036A	0.037A

5.2 For KVL:

	theoretical	practical
V_1 (V)	1V	1.2V
V_2 (V)	2.2V	2.1V
V_3 (V)	1.8V	1.7V
V(V)	0.1V	0.1V

6 Result

For KCL, total input current is equal to total output current at node A.
For KVL, the net potential in a loop is zero