

Lab Report: Half-Wave Rectifier Experiment

ee23BTech11016

Aim

To build a Half Wave Rectifier

Apparatus

- AC power supply
- Diode
- Resistor ($R_{\text{load}} = 1 \text{ k}\Omega$)
- Capacitor ($C_{\text{filter}} = 1 \mu\text{F}$) [Filter]
- Oscilloscope
- Multimeter
- Connecting wires

Circuit Diagrams

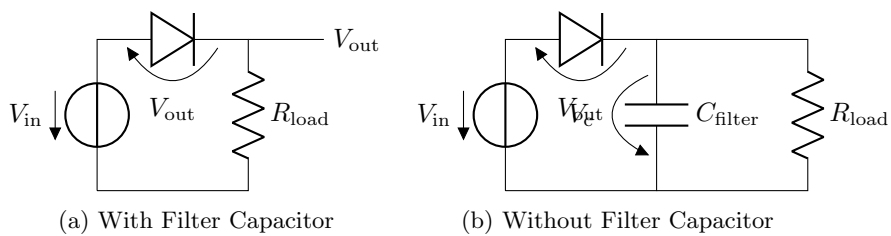


Figure 1: Half-Wave Rectifier Circuit Diagrams

Theory

1. A half-wave rectifier is a simple electronic circuit that converts alternating current (AC) to direct current (DC).
2. The basic principle behind a half-wave rectifier is to allow only one half-cycle of the AC waveform to pass through, resulting in a pulsating DC output.
3. During the positive half-cycle of the AC input voltage, the diode conducts and allows current to flow through the load.
4. However, during the negative half-cycle, the diode blocks the current, resulting in no output.

Procedure

1. Set up the circuit as shown in Figure ?? or Figure ??.
2. Connect the oscilloscope to measure the input and output waveforms.
3. Gradually increase the AC voltage and record the readings.
4. Measure the output DC voltage and ripple using a multimeter.

Calculation

Output Voltage Calculation

The output voltage (V_{out}) of the half-wave rectifier can be calculated using the formula mentioned in the theory section:

$$\begin{aligned} V_{\text{out}} &= V_{\text{max}} \cdot \frac{T}{2\pi} \cdot \left(1 - \cos\left(\frac{2\pi t}{T}\right) \right) \\ &= \\ &= \end{aligned} \tag{1}$$

Where:

V_{max} : Peak value of the AC input voltage

T : Period of the AC input waveform

t : Time

Average Output Voltage

The average output voltage (V_{avg}) can be calculated by integrating V_{out} over one complete cycle and dividing by the period T :

$$\begin{aligned} V_{\text{avg}} &= \frac{1}{T} \int_0^T V_{\text{out}} dt \\ &= \\ &= \end{aligned} \tag{2}$$

[Include the integration steps and final result.]

Ripple Factor

The ripple factor (γ) is a measure of the AC component in the rectified output and can be calculated using the formula:


$$\begin{aligned} \gamma &= \frac{\sqrt{\frac{1}{T} \int_0^T (V_{\text{out}} - V_{\text{avg}})^2 dt}}{V_{\text{avg}}} \\ &= \\ &= \end{aligned} \tag{3}$$

Observations

During the experiment, the following observations were made:

1. **Input Voltage (V_{in}):**
2. **Output Voltage (V_{out}):**
3. **Ripple Voltage:**
4. **Filter Capacitor Voltage (V_c):**
5. **Load Resistor Voltage (V_{load}):**

Lab Status

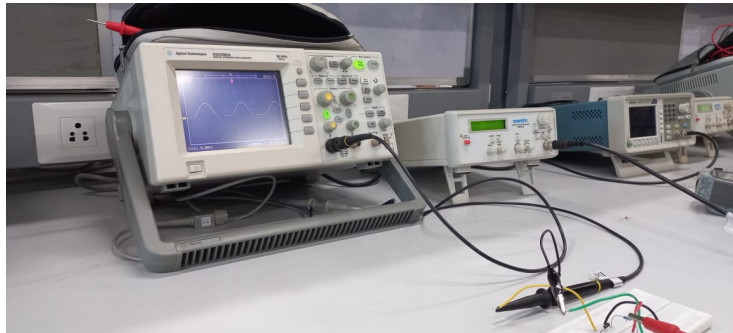

Conclusion

In conclusion, the half-wave rectifier is a fundamental circuit for converting AC to DC. While simple and cost-effective, its limitations in efficiency and output quality make it suitable for specific low-power applications.